

# **Type system for automated generation of reversible circuits**

Benoît Valiron, PPS, Paris Diderot, France


TYPES 2014

# Plan of the talk

- Reversible circuits.
- Compiling a PCF-like language into reversible circuits.
- The proposed type system.
- Future Work.
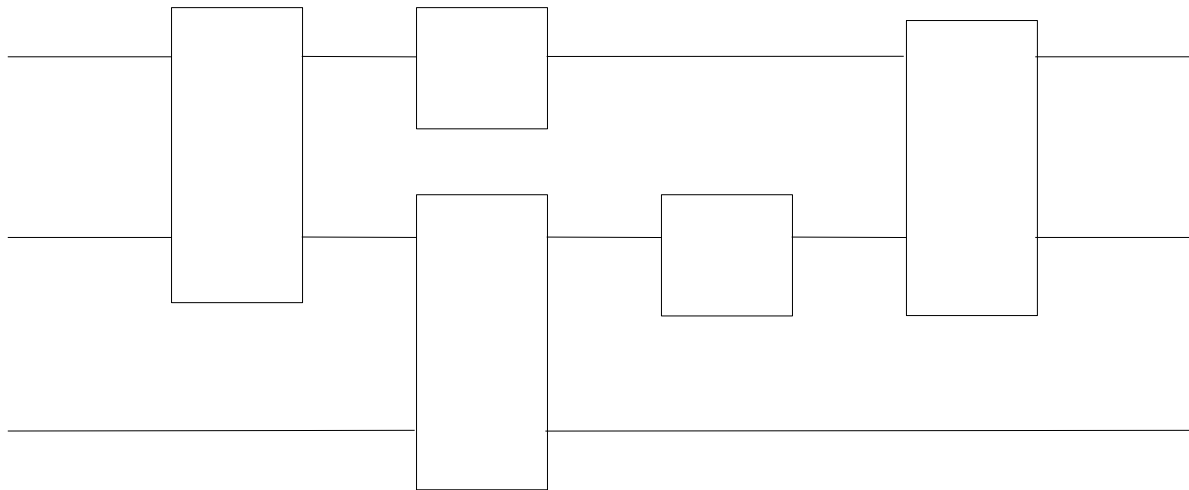
# Reversible circuits

- Booleans flow on wires from left to right;
- gates modifies the booleans as they moved through;
- gates are “reversible”: to reverse, have the time flow backward;
- no loops, no conditional escape.




- Very useful as quantum oracles.


# The building blocks




# The building blocks

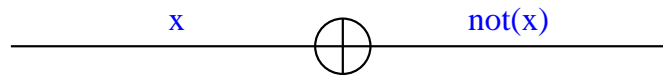


# The building blocks

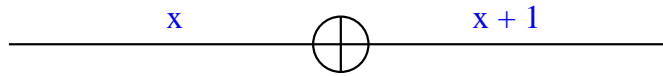

# The building blocks

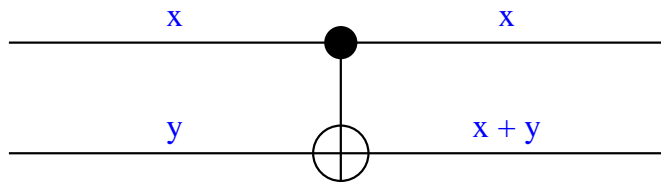


# The building blocks

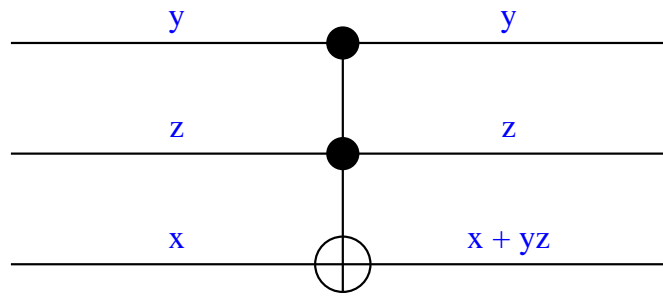





# The building blocks

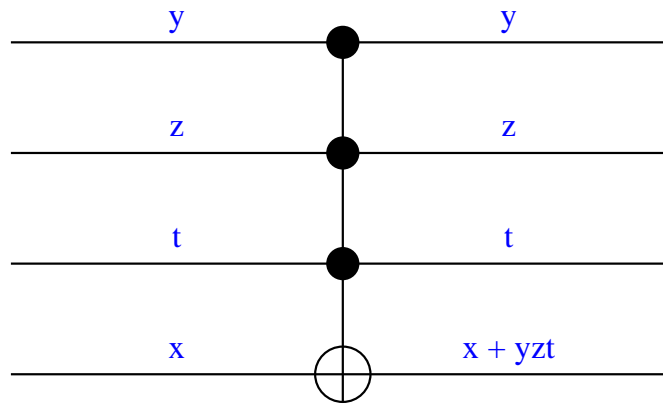


# The building blocks

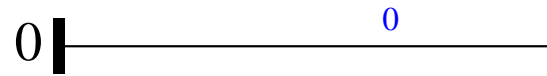

# They can be combined

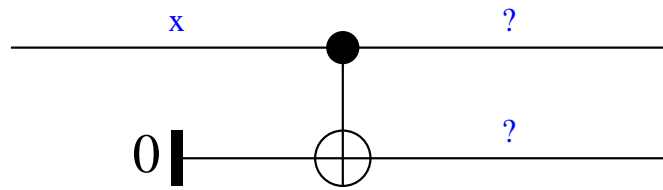

# They can be combined

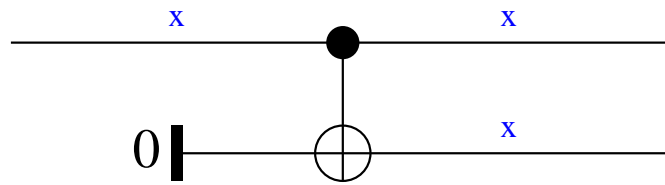

# The problem


A circuit is a linear list of gates (no loop!).

Given a function  $\{0, 1\}^n \rightarrow \{0, 1\}^m$ , can you find a circuit that “compute” the function?

Hopefully as automatically as possible as quantum oracles can be quite large and complex.
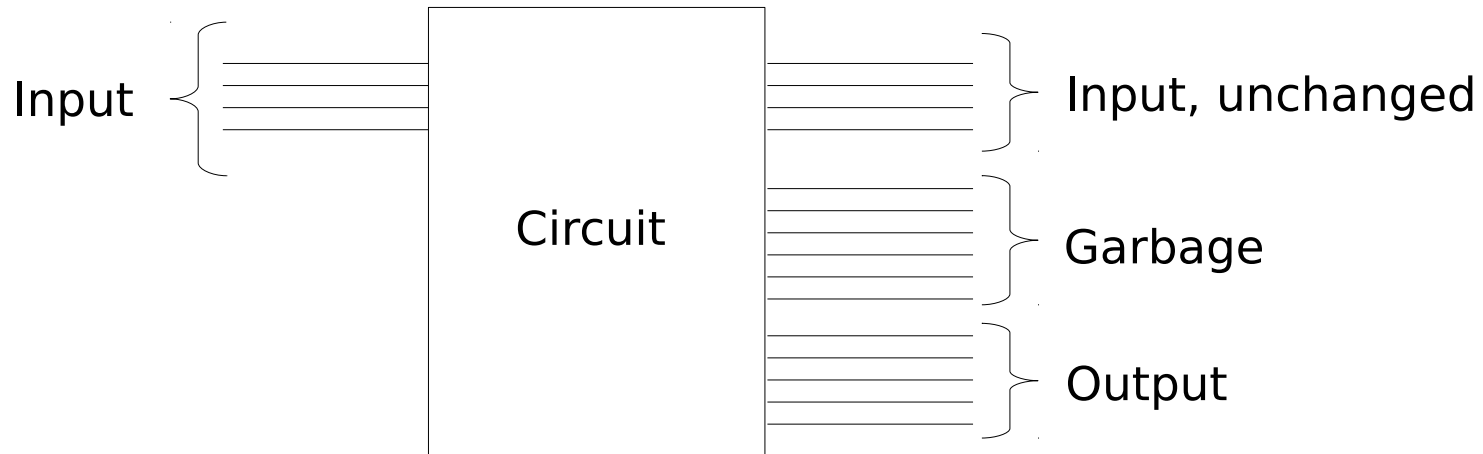
# A compositional approach

Landauer embeddings: circuits of the form




computing  $f : \text{Input} \longrightarrow \text{Output}$ .

# A compositional approach

Landauer embeddings can be composed



$$x \xrightarrow{f} f(x) \xrightarrow{g} g(f(x))$$

corresponds to

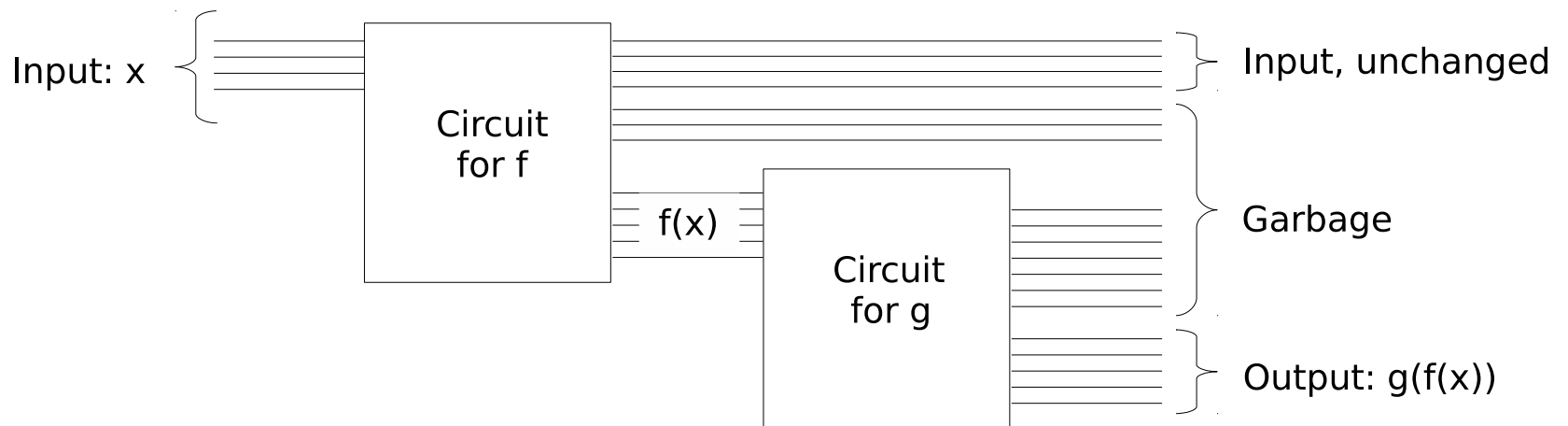
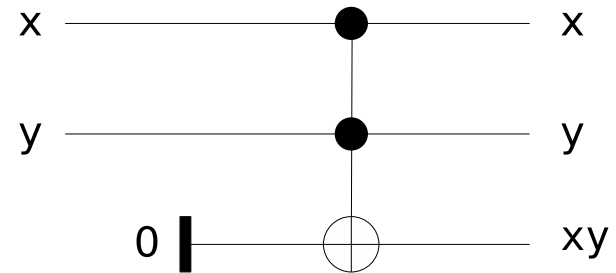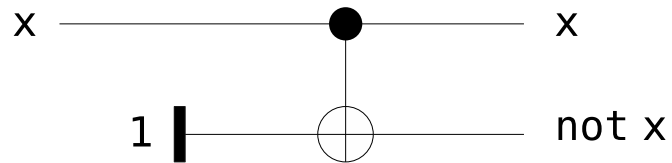
# A compositional approach

Two elementary Landauer embeddings for not and and:






# A compositional approach

Example: the disjunction

$$(x, y) \mapsto \text{not} (\text{and} (\text{not } x) (\text{not } y))$$

gives the circuit

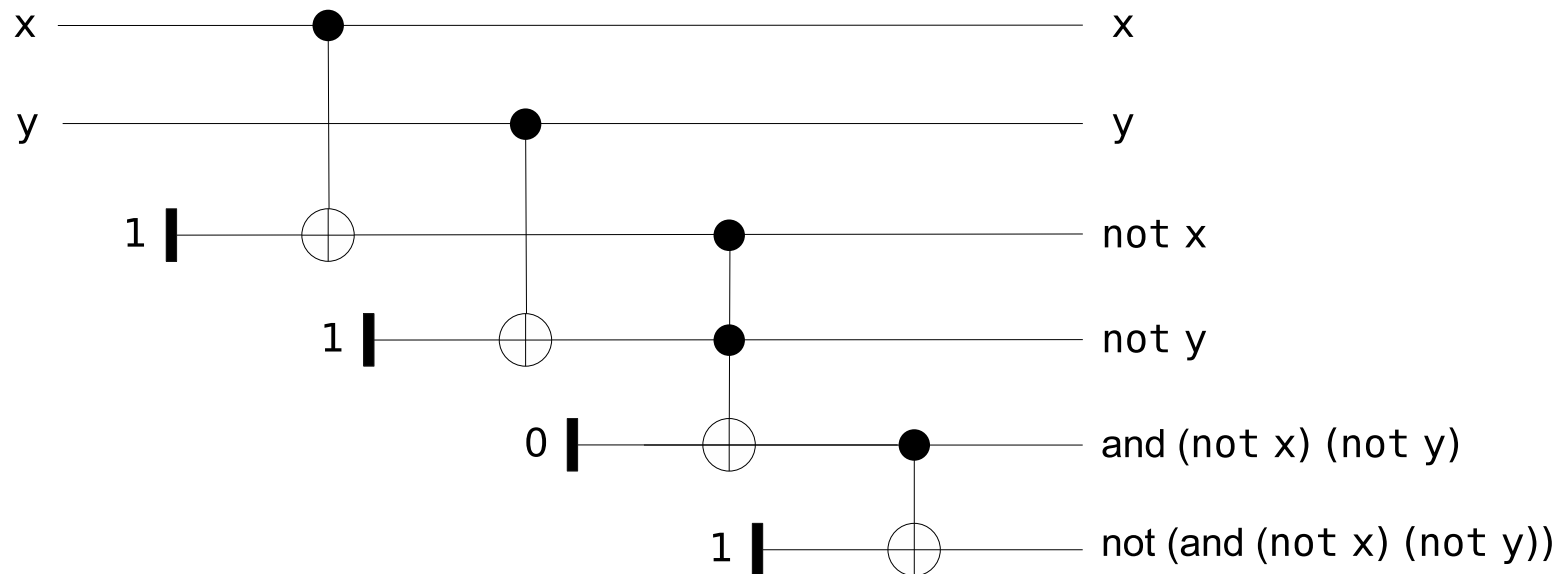

# Circuits as operational semantics

Consider a lambda-calculus

$$M, N ::= x \mid \lambda x.M \mid MN \mid \text{and} \mid \text{not} \mid \dots$$
$$A, B ::= \text{bit} \mid A \rightarrow B$$

An abstract machine is

$$(C, L, M)$$

- $C$ : a circuit;
- $M$ : a term;
- $L$ : a function mapping free variables (of type `bit`) of  $M$  to wires.

# Circuits as operational semantics

Example: the abstract machine for the term

$$x, y : \text{bit} \vdash (((\lambda z. \lambda t. \lambda s. s (\text{and } t z)) (\text{not } x)) (\text{not } y)) \text{not} : \text{bit}$$

is initialized with

$$M = (((\lambda z. \lambda t. \lambda s. s (\text{and } t z)) (\text{not } x)) (\text{not } y)) \text{not}$$

$C$  is

———  $x$   
———  $y$

# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = (((\lambda z.\lambda t.\lambda s.s \text{ (and } t \ z))(\text{not } x))(\text{not } y)) \text{not}$

$C$  is

———  $x$

———  $y$

# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = (((\lambda z.\lambda t.\lambda s.s \text{ (and } t \ z))(\text{not } x))(\text{not } y)) \text{ not}$

$C$  is

———  $x$


———  $y$

# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = (((\lambda z.\lambda t.\lambda s.s \text{ (and } t \ z)) \ z_1)(\text{not } y)) \text{not}$

$C$  is

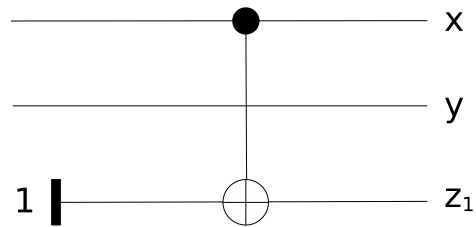


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = (((\lambda z. \lambda t. \lambda s. s \text{ (and } t \ z)) \ z_1) (\text{not } y)) \text{not}$

$C$  is

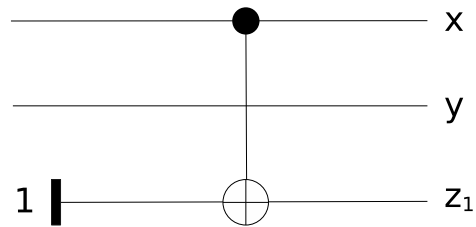


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = ((\lambda t.\lambda s.s (\text{and } t \ z_1))(\text{not } y)) \text{not}$

$C$  is

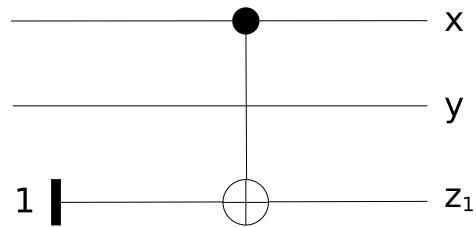




# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = ((\lambda t.\lambda s.s (\text{and } t z_1))(\text{not } y)) \text{not}$

$C$  is

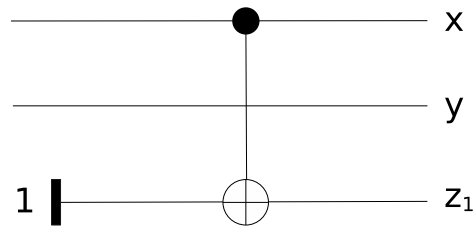


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = ((\lambda t. \lambda s. s \text{ (and } t \ z_1)) \ z_2) \text{ not}$

$C$  is

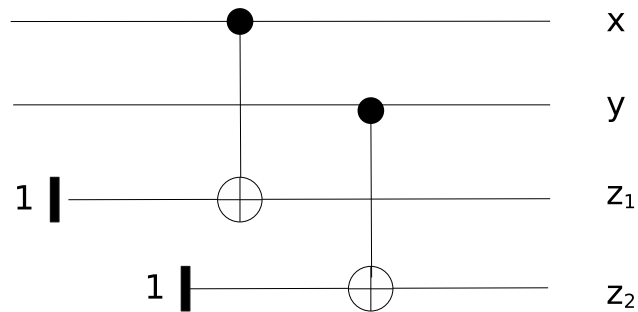


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = ((\lambda t. \lambda s. s \text{ (and } t \ z_1)) \ z_2) \text{ not}$

$C$  is

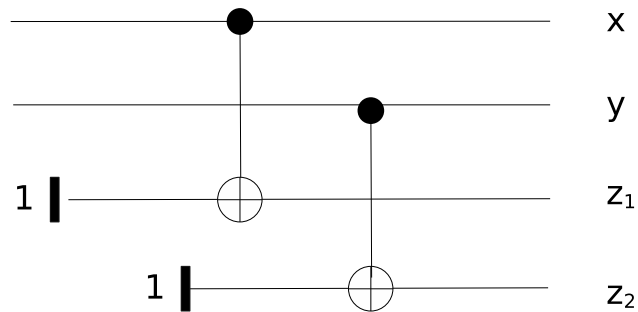


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = (\lambda s.s (\text{and } z_2 z_1)) \text{ not}$

$C$  is

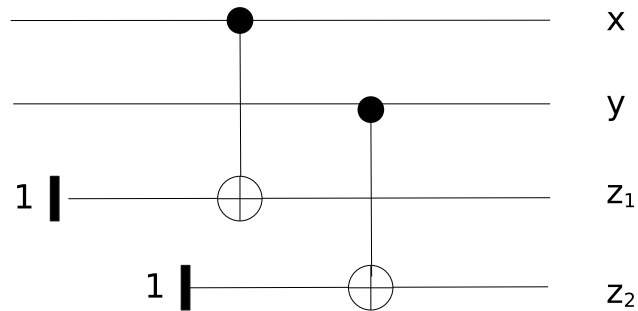


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = (\lambda s.s (\text{and } z_2 z_1)) \text{ not}$

$C$  is

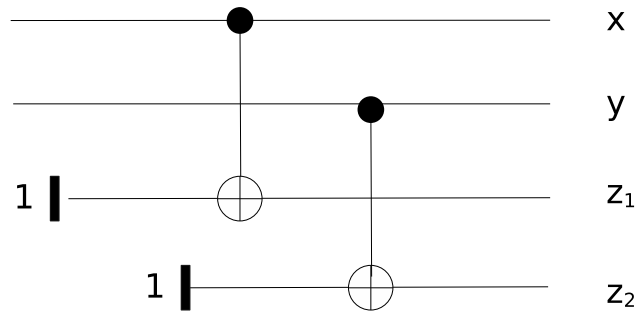


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = \text{not}(\text{and } z_2 \ z_1)$

$C$  is

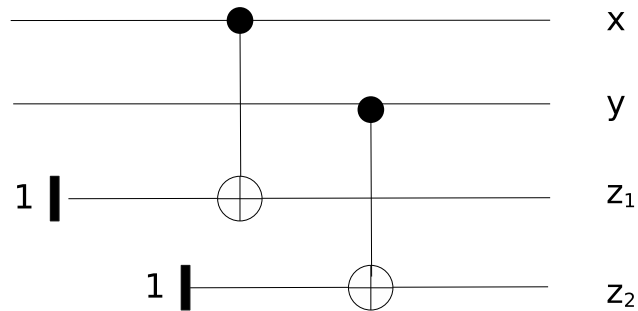


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = \text{not } (\text{and } z_2 \ z_1)$

$C$  is

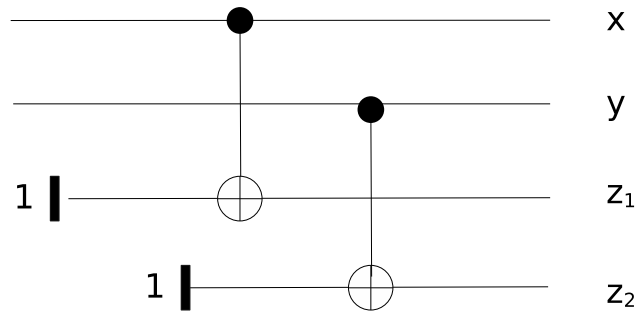


# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = \text{not } z_3$

$C$  is

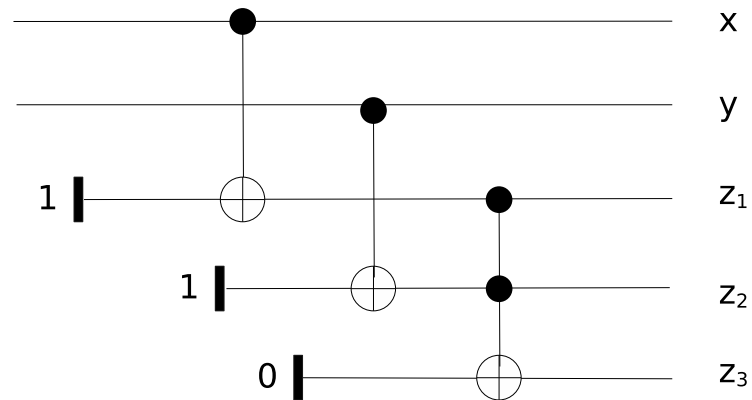




# Circuits as operational semantics

Evaluating the machine in call-by-value...

$M = \text{not } z_3$

$C$  is

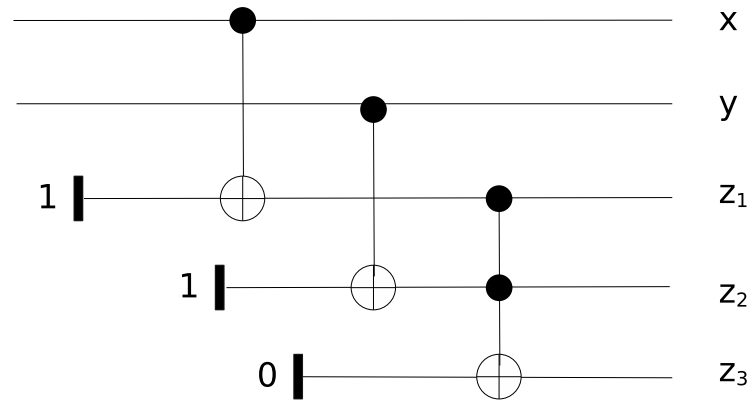


# Circuits as operational semantics


Evaluating the machine in call-by-value...

$M = z_4$

$C$  is

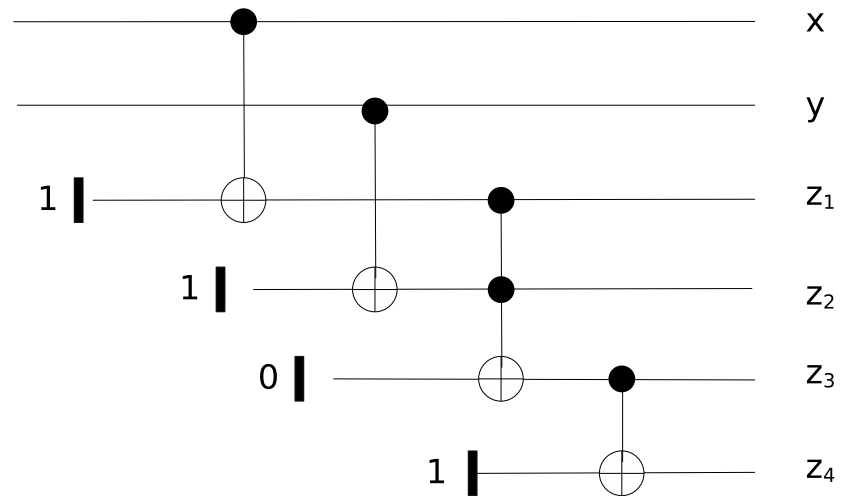


# Circuits as operational semantics

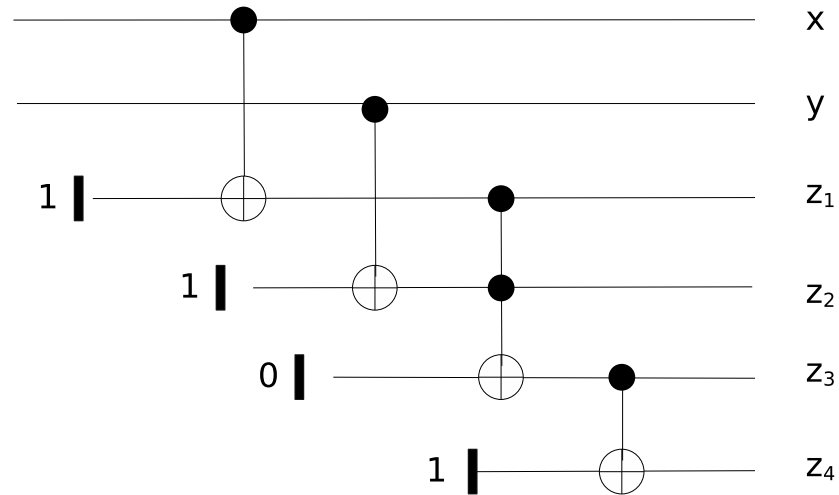


Note:

- this is the same circuit for  $\text{not}(\text{and}(\text{not } x)(\text{not } y))$ ,
- the wire  $z_3$  is not visible to the program.

# Verbosity

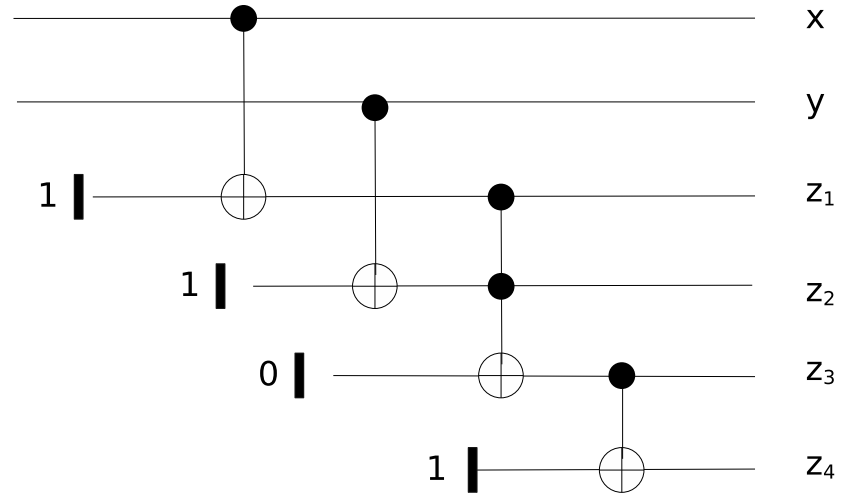


can then be replaced with

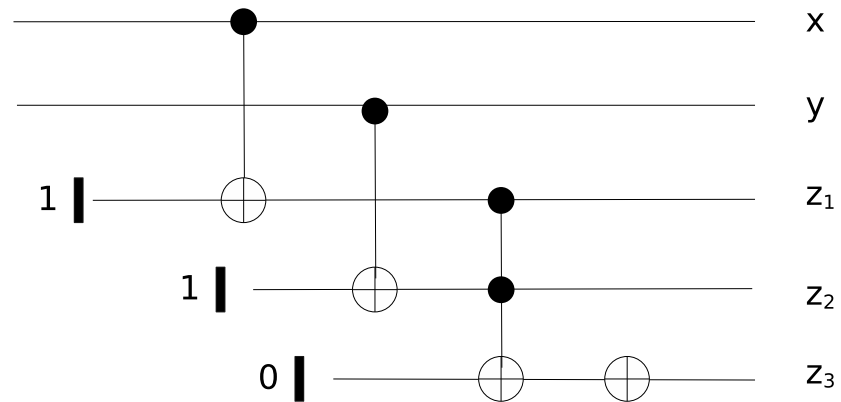

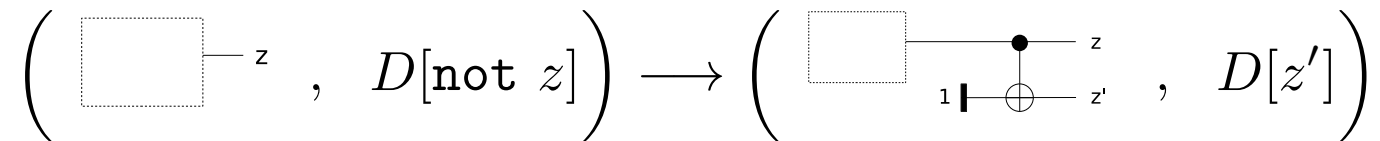
# Verbosity

In general, if  $D[-]$  is in evaluation position:

- If the wire  $z$  is used more than once in the program



- Else:

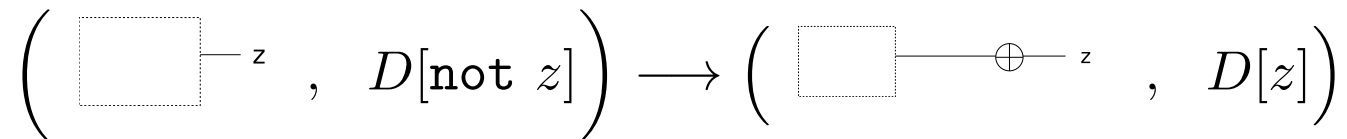

Easy to track for `not (and (not  $x$ ) (not  $y$ ))`,

not so much for `(((( $\lambda z.\lambda t.\lambda s.s$  (and  $t z$ ))(not  $x$ ))(not  $y$ )) not.`


# Typing wires

The problem comes from the fact that wire occupancy by a control is not monitored. Types can be used for that purpose.

Idea: Wires are described as sorts for the type `bit`, and sorts are themselves typed with the “occupancy level” of the wire.

$$M, N ::= x \mid \lambda x.M \mid MN \mid \text{and} \mid \text{not}_\alpha \dots$$
$$A, B ::= \alpha \mid A \rightarrow B$$
$$\tau ::= 0 \mid 1 \mid +.$$

and sorts enjoy a transitive relation:

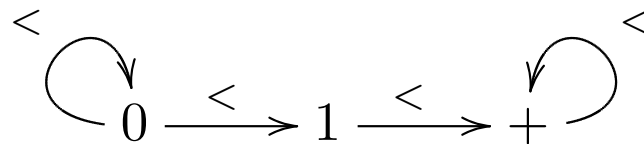

# Typing wires

$$\alpha_1 : \tau_1 \dots \alpha_n : \tau_n \mid x_1 : A_1 \dots x_m : A_m \vdash M : B$$

$$\frac{|\Delta| = |A|}{\Delta \mid x : A \vdash x : A} \quad \frac{\Delta \mid \Gamma, x : A \vdash M : B}{\Delta \mid \Gamma \vdash \lambda x.M : A \rightarrow B} \quad \frac{\Gamma_1 \mid \Delta \vdash N : A \quad \Gamma_2 \mid \Delta \vdash M : A \rightarrow B}{\Gamma_1 \cup \Gamma_2 \mid \Delta \vdash MN : B}$$

(plus weakening) where

$$\begin{aligned} & (\alpha_1 : \tau_1 \dots \alpha_n : \tau_n, \beta_1 : \sigma_1 \dots \beta_m : \sigma_m) \cup \\ & (\alpha_1 : \tau'_1 \dots \alpha_n : \tau'_n, \beta_{m+1} : \sigma_{m+1} \dots \beta_k : \sigma_k) \\ = & (\alpha_1 : \max(\tau_1, \tau'_1) \dots \alpha_n : \max(\tau_n, \tau'_n), \beta_1 : \sigma_1 \dots \beta_k : \sigma_k) \end{aligned}$$

with  $\max(\tau, \tau') = \min(\sigma \mid \tau, \tau' \leq \sigma, \sigma > \tau \text{ or } \sigma > \tau')$ .

# Typing wires

Example:

$$\frac{\alpha : 0 \mid x : \alpha \vdash M : A \rightarrow B \quad \alpha : 0 \mid x : \alpha \vdash N : A}{\alpha : \max(0, 0) \mid x : \alpha \vdash MN : B}$$



# Typing wires

Example:

$$\frac{\alpha : 0 \mid x : \alpha \vdash M : A \rightarrow B \quad \alpha : 0 \mid x : \alpha \vdash N : A}{\alpha : 0 \mid x : \alpha \vdash MN : B}$$

Since  $0 \leq 0$  and  $0 > 0$ .

That is, the wire  $\alpha$  is not used in the circuit generated by  $MN$ .

# Typing wires

Example:

$$\frac{\alpha : 1 \mid x : \alpha \vdash M : A \rightarrow B \quad \alpha : 0 \mid x : \alpha \vdash N : A}{\alpha : \max(1, 0) \mid x : \alpha \vdash MN : B}$$

# Typing wires

Example:

$$\frac{\alpha : 1 \mid x : \alpha \vdash M : A \rightarrow B \quad \alpha : 0 \mid x : \alpha \vdash N : A}{\alpha : 1 \mid x : \alpha \vdash MN : B}$$

Since  $0, 1 \leq 1$  and  $1 > 0$ .

That is, the wire  $\alpha$  is used only once in the circuit generated by  $MN$ .

# Typing wires

Example:

$$\frac{\alpha : 1 \mid x : \alpha \vdash M : A \rightarrow B \quad \alpha : 1 \mid x : \alpha \vdash N : A}{\alpha : \max(1, 1) \mid x : \alpha \vdash MN : B}$$

# Typing wires

Example:

$$\frac{\alpha : 1 \mid x : \alpha \vdash M : A \rightarrow B \quad \alpha : 1 \mid x : \alpha \vdash N : A}{\alpha : \quad + \quad \mid x : \alpha \vdash MN : B}$$

Since  $1 \leq +$ ,  $1 \not\leq 1$  and  $+ > 1$ .

The wire  $\alpha$  is used more than once in the circuit generated by  $MN$ .

# Types and constant terms

$$\frac{\tau_1 \geq 1}{\alpha : \tau_1, \beta : \tau_2 \mid \emptyset \vdash \mathbf{not}_\alpha : \alpha \rightarrow \beta}$$

$$\frac{\tau_1, \tau_2 \geq 1}{\alpha : \tau_1, \beta : \tau_2, \gamma : \tau_3 \mid \emptyset \vdash \mathbf{and} : \alpha \rightarrow \beta \rightarrow \gamma}$$

# Using types in the reduction

Suppose that  $\Delta, \beta : \tau \mid \Gamma \vdash M : \alpha$ , and that  $M = D[\text{not}_\beta z]$  is in evaluation position.

- If  $\tau = +$ , then

$$\left( \boxed{\phantom{z}}^z, D[\text{not}_\beta z] \right) \longrightarrow \left( \boxed{\phantom{z}} \begin{array}{c} \text{---} \bullet \text{---} z \\ | \\ \text{---} \oplus \text{---} z' \\ | \\ \text{---} 1 \text{---} \end{array}, D[z'] \right)$$

- Else:

$$\left( \boxed{\phantom{z}}^z, D[\text{not}_\beta z] \right) \longrightarrow \left( \boxed{\phantom{z}} \text{---} \oplus \text{---} z, D[z] \right)$$

# Revisiting the example


Both of the terms  $\text{not}_\epsilon (\text{and} (\text{not}_\alpha x) (\text{not}_\beta y))$

and  $(((\lambda z. \lambda t. \lambda s. s (\text{and } t z)) (\text{not}_\alpha x)) (\text{not}_\beta y)) \text{not}_\epsilon$

can be typed with the context

$$\dots, \alpha : +, \beta : +, \epsilon : 1, \gamma : 0 \mid x : \alpha, y : \beta \vdash - : \gamma$$

and the circuit is

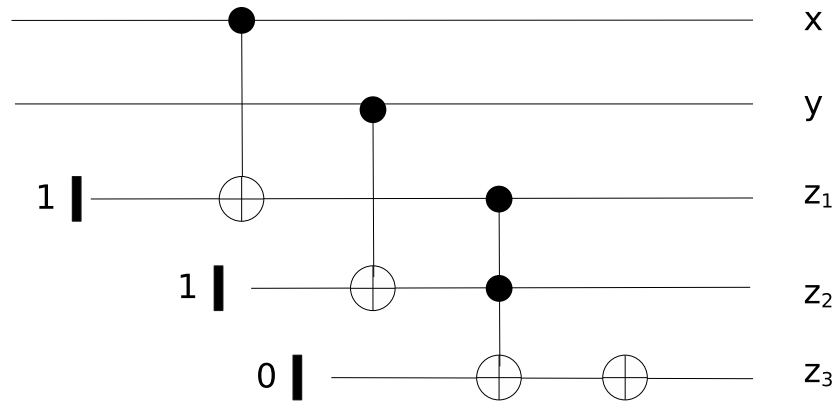



## Revisiting the example


Both of the terms  $\text{not}_\epsilon (\text{and} (\text{not}_\alpha x) (\text{not}_\beta y))$

and  $(((\lambda z. \lambda t. \lambda s. s (\text{and } t z)) (\text{not}_\alpha x)) (\text{not}_\beta y)) \text{not}_\epsilon$

can also be typed with the context

$$\dots, \alpha : 1, \beta : 1, \epsilon : 1, \gamma : 0 \mid x : \alpha, y : \beta \vdash - : \gamma$$

and the circuit is instead

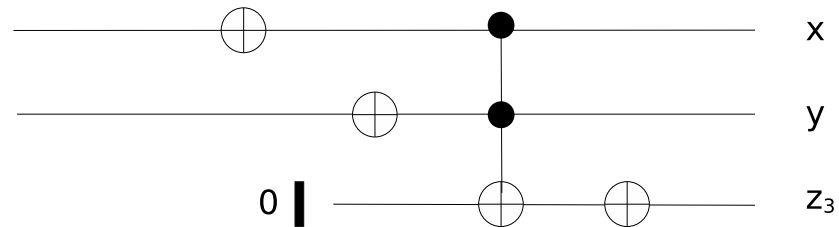

but note that we use the fact that  $x$  and  $y$  are only used once each.

# The result

For a function  $x_1 : \text{bit}, \dots, x_n : \text{bit} \vdash M : \text{bit}$ , we therefore have three operational semantics:

- Regular call-by-value beta-reduction when  $x_1 \dots x_n$  are fed with concrete booleans.
- Verbose circuit-generation.
- Smart circuit-generation.

They all correspond to the same boolean function, and the verbose circuit is obviously always larger than the smart one.

# Conclusion and future steps

- A step towards automation in the design of quantum oracle.
- Possible extensions:
  - parametricity in wire naming;
  - lists (e.g. of bits);
  - in general: complete PCF.
- It does not however capture all possible optimizations:
  - eta-conversion (code factorization);
  - evaluation of constants (e.g. `not true`).
- How to measure "smartness" ?